

Engineering
and
Architecture
Analog
Electronics
Fundamentals
EEE223

Lec 7

Diode Limiters and Clampers


Lecturer Sally Adil


Clippers

- Diode circuits, called limiters or clippers, are sometimes used to clip off portions of signal voltages above or below certain levels.
- Figure shows a diode positive **limiter** (also called **clipper**) that limits or clips the positive part of the input voltage. As the input voltage goes positive, the diode becomes forward biased and conducts current. Point A is limited to +0.7 V when the input voltage exceeds this value. value.


-
- When the input voltage goes back below 0.7 V, the diode is reverse-biased and appears as an open. The output voltage looks like the negative part of the input voltage, but with a magnitude determined by the voltage divider formed by R_1 and the load resistor, R_L , as follows:

$$V_{out} = \left(\frac{R_L}{R_1 + R_L} \right) V_{in}$$

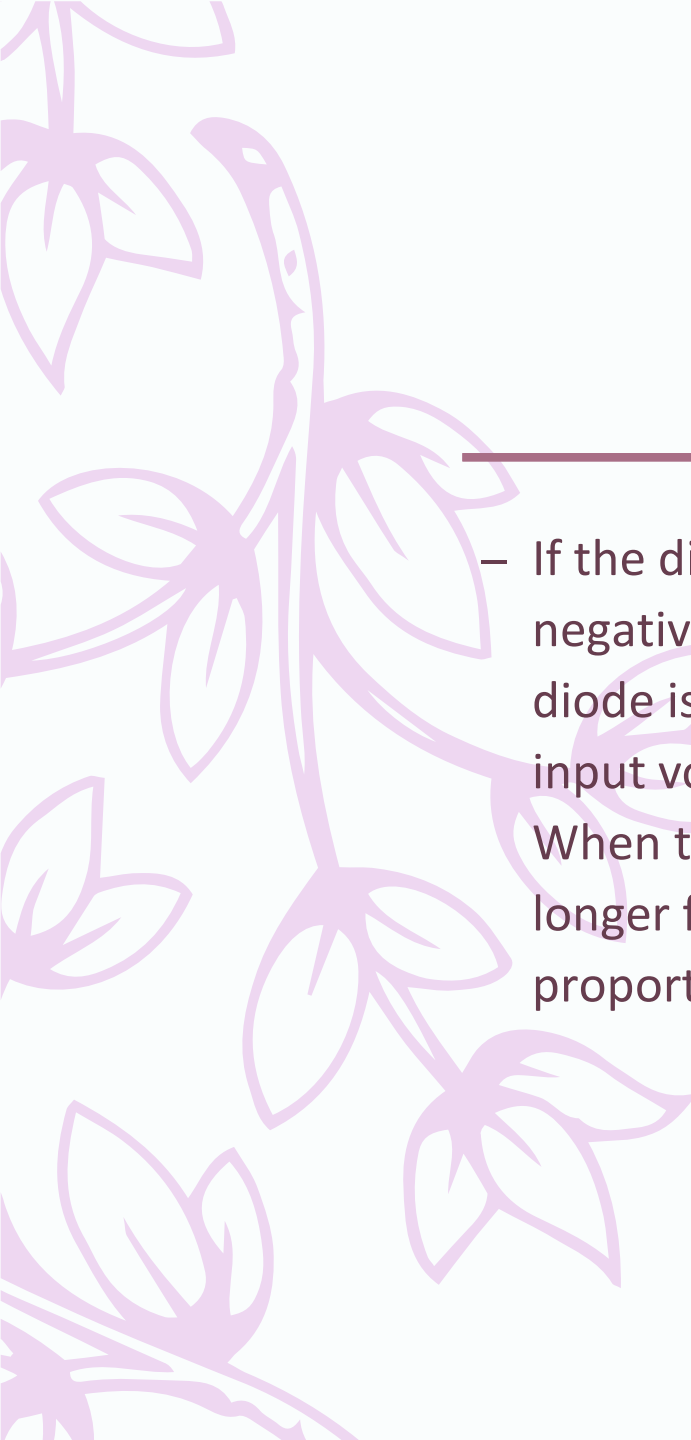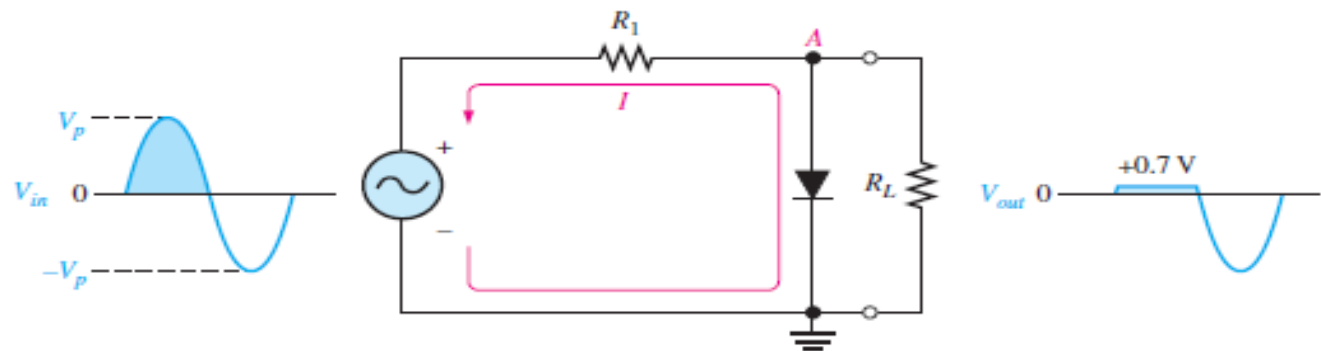- 
-
- If the diode is turned around, as in Figure 2–52(b), the negative part of the input voltage is clipped off. When the diode is forward-biased during the negative part of the input voltage, point *A* is held at -0.7 V by the diode drop. When the input voltage goes above -0.7 V , the diode is no longer forward-biased; and a voltage appears across *RL* proportional to the input voltage.



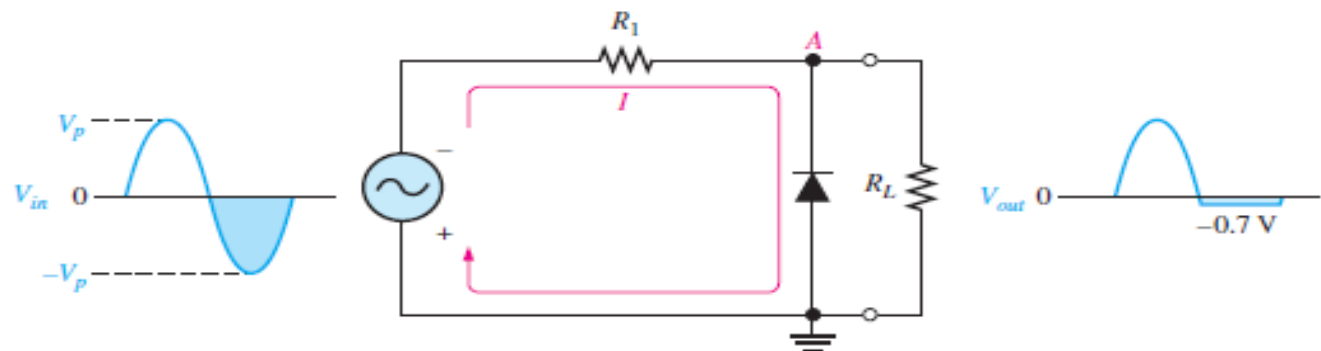
(a) Limiting of the positive alternation. The diode is forward-biased during the positive alternation (above 0.7 V) and reverse-biased during the negative alternation.



(b) Limiting of the negative alternation. The diode is forward-biased during the negative alternation (below -0.7 V) and reverse-biased during the positive alternation.

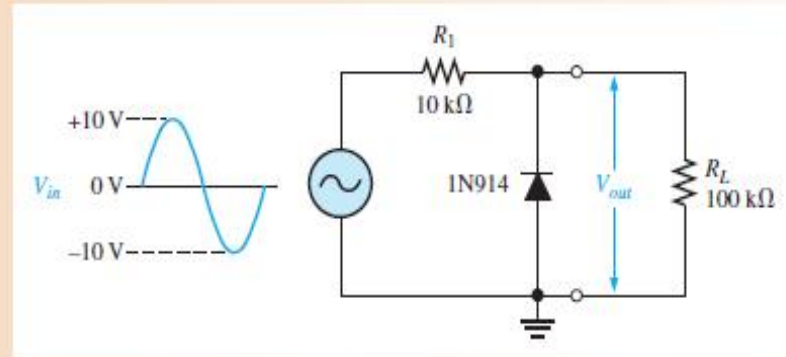EXAMPLE 2-10

What would you expect to see displayed on an oscilloscope connected across R_L in the limiter shown in Figure 2-53?




► **FIGURE 2-53**

Solution

The diode is forward-biased and conducts when the input voltage goes below -0.7 V . So, for the negative limiter, determine the peak output voltage across R_L by the following equation:

$$V_{p(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{p(in)} = \left(\frac{100\text{ k}\Omega}{110\text{ k}\Omega} \right) 10\text{ V} = 9.09\text{ V}$$

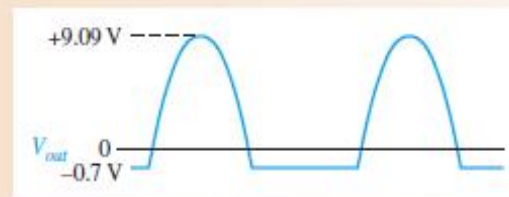The scope will display an output waveform as shown in Figure 2-54.




► **FIGURE 2-54**

Output voltage waveform for Figure 2-53.


Biased Limiters


- The level to which an ac voltage is limited can be adjusted by adding a bias voltage, V_{BIAS} , in series with the diode.
- The voltage at point A must equal $V_{BIAS} + 0.7\text{ V}$ before the diode will become forward-biased and conduct.
- Once the diode begins to conduct, the voltage at point A is limited to $V_{BIAS} + 0.7\text{ V}$ so that all input voltage above this level is clipped off.


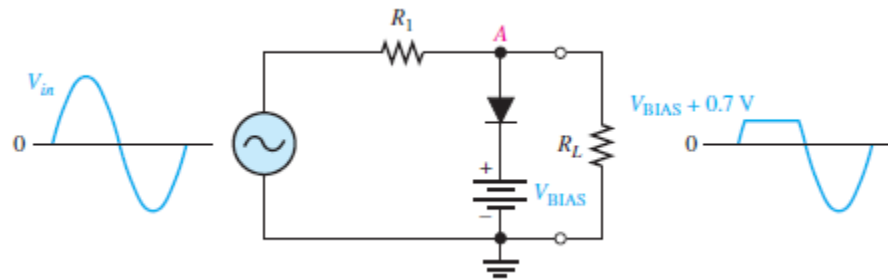


Negative Limiters:

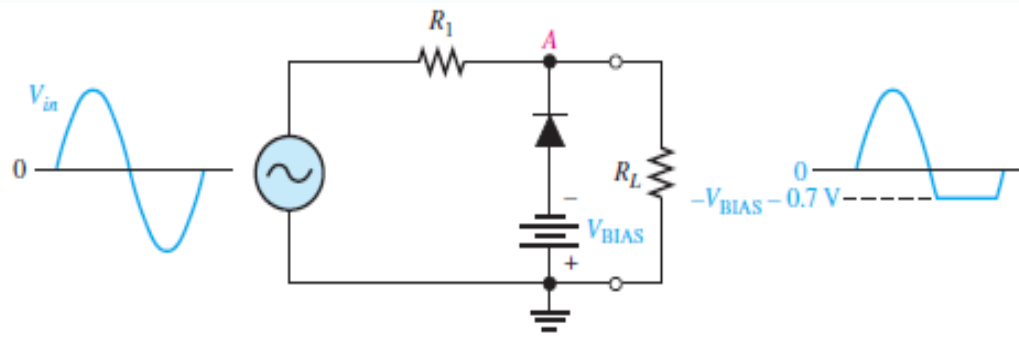- To limit a voltage to a specified negative level, the diode and bias voltage must be connected as in Figure. In this case, the voltage at point A must go below $-V_{BIAS} - 0.7\text{ V}$ to forward-bias the diode and initiate limiting action as shown.



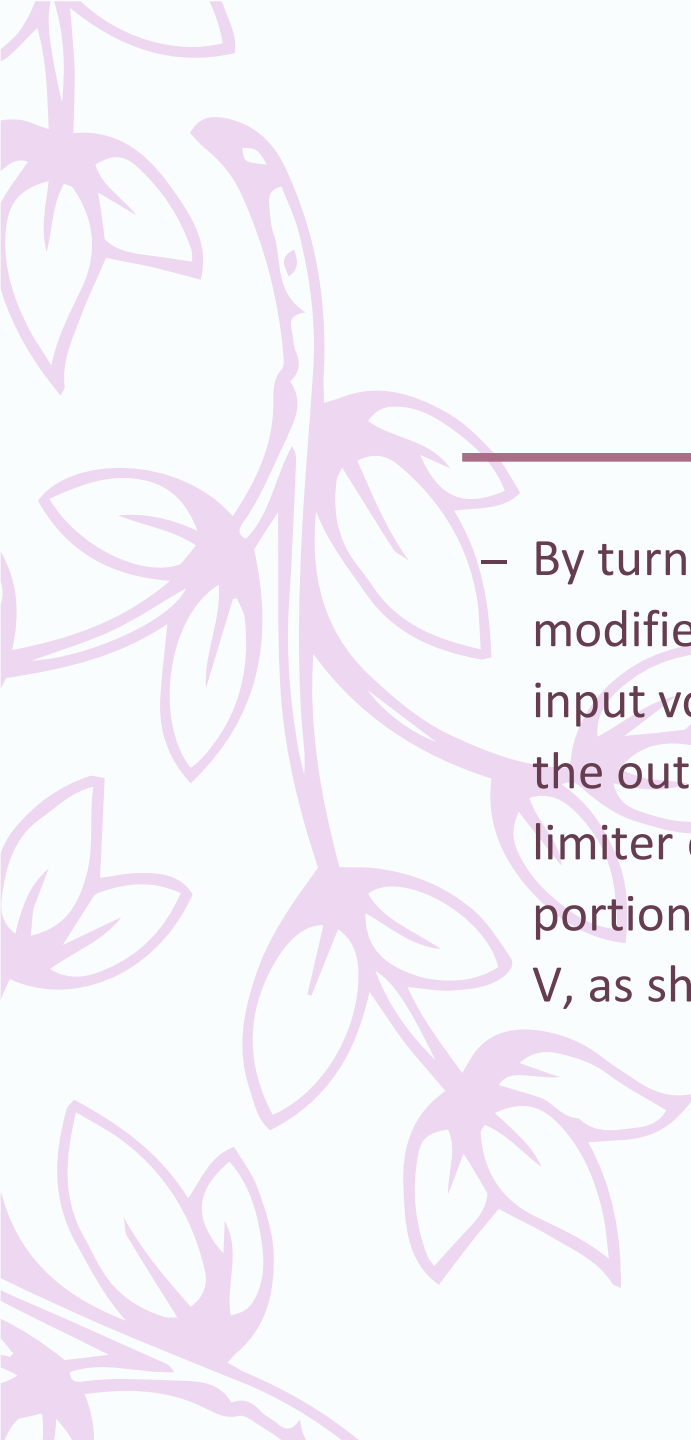
- 
-
- By turning the diode around, the positive limiter can be modified to limit the output voltage to the portion of the input voltage waveform above $V_{BIAS} - 0.7\text{ V}$ as shown by the output waveform in Figure (a). Similarly, the negative limiter can be modified to limit the output voltage to the portion of the input voltage waveform below $-V_{BIAS} + 0.7\text{ V}$, as shown by the output waveform in part (b).

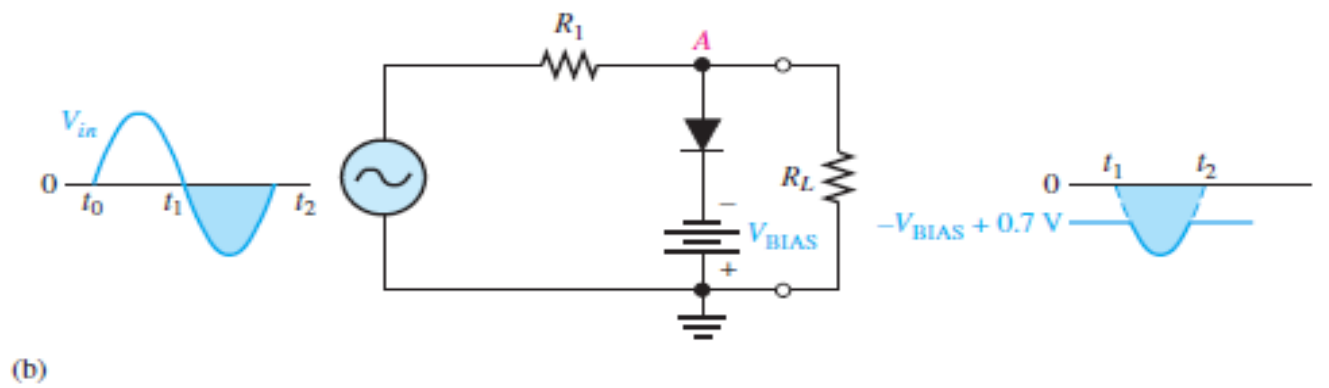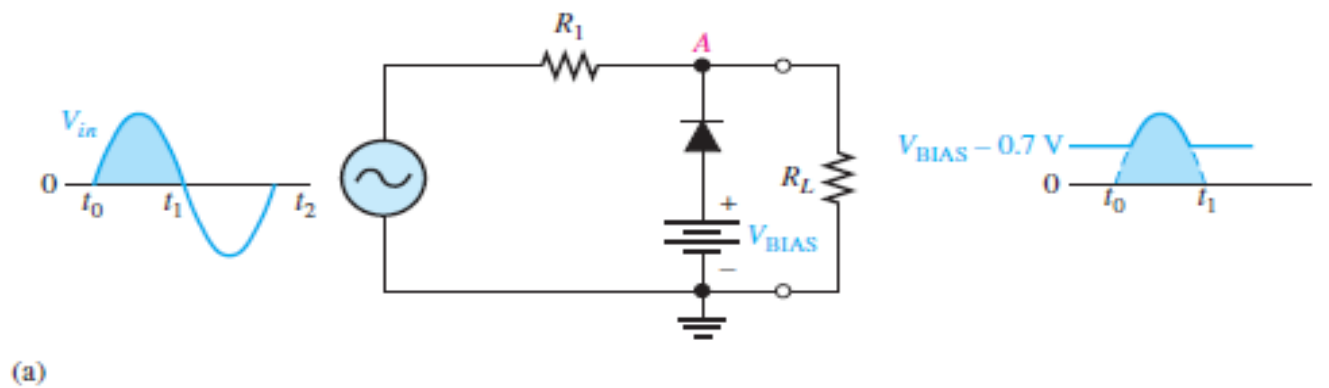

EXAMPLE 2-11

Figure 2-58 shows a circuit combining a positive limiter with a negative limiter. Determine the output voltage waveform.


► FIGURE 2-58

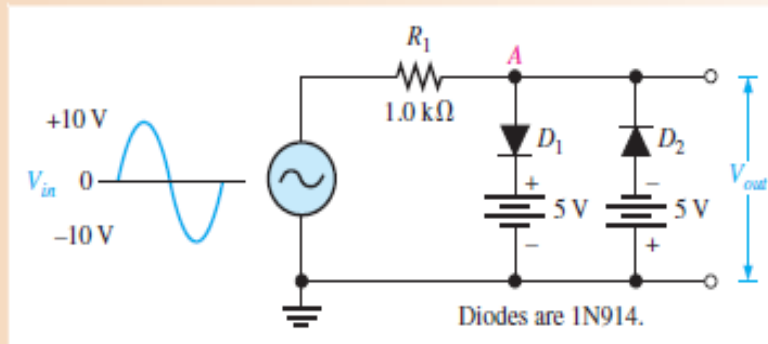


Solution When the voltage at point *A* reaches +5.7 V, diode D_1 conducts and limits the waveform to +5.7 V. Diode D_2 does not conduct until the voltage reaches -5.7 V. Therefore, positive voltages above +5.7 V and negative voltages below -5.7 V are clipped off. The resulting output voltage waveform is shown in Figure 2-59.

► FIGURE 2-59


Output voltage waveform for Figure 2-58.

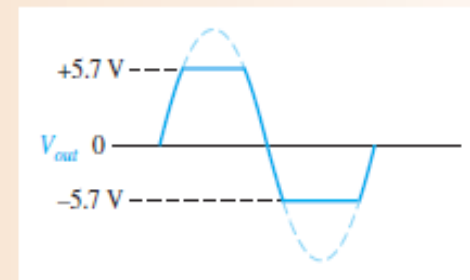


Related Problem Determine the output voltage waveform in Figure 2-58 if both dc sources are 10 V and the input voltage has a peak value of 20 V.

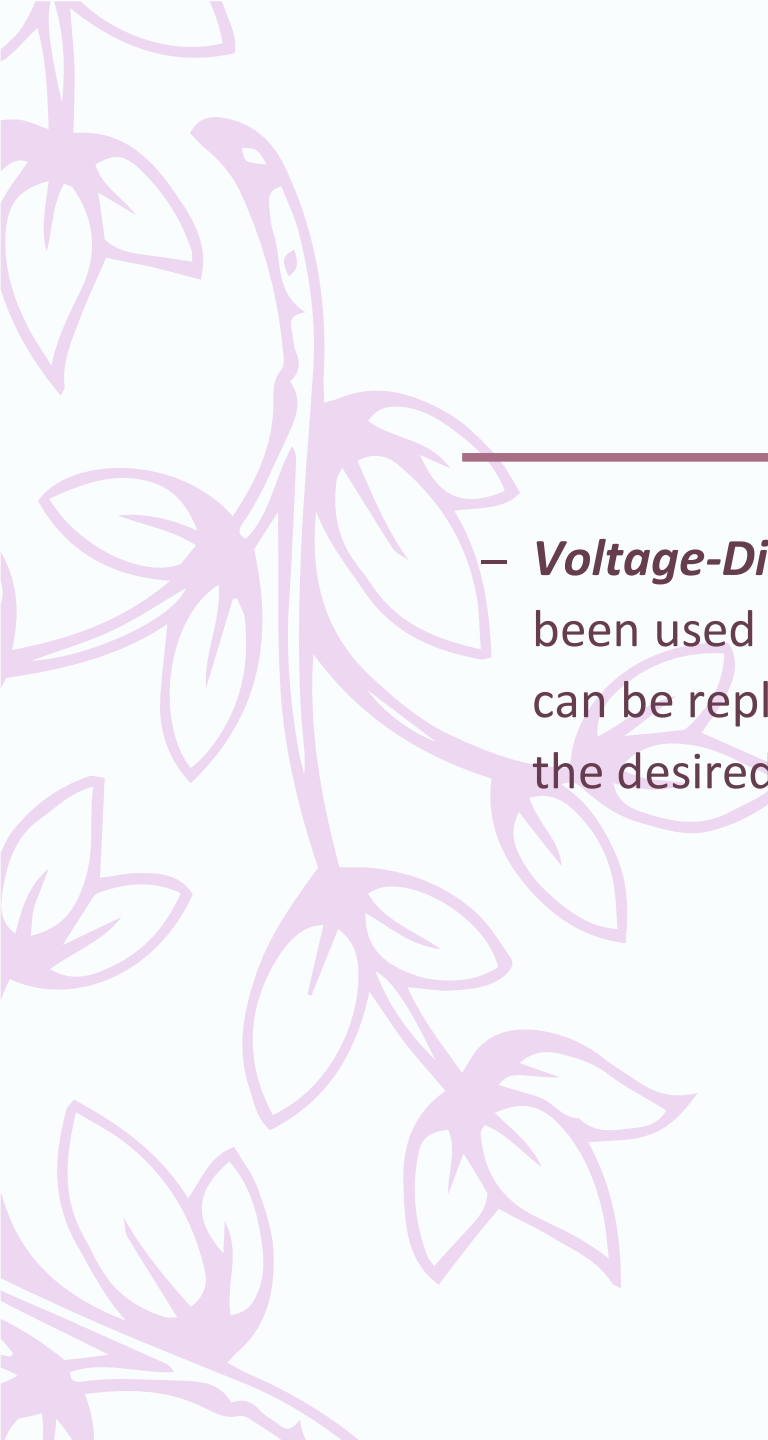- 
-
- ***Voltage-Divider Bias*** The bias voltage sources that have been used to illustrate the basic operation of diode limiters can be replaced by a resistive voltage divider that derives the desired bias voltage from the dc supply voltage.

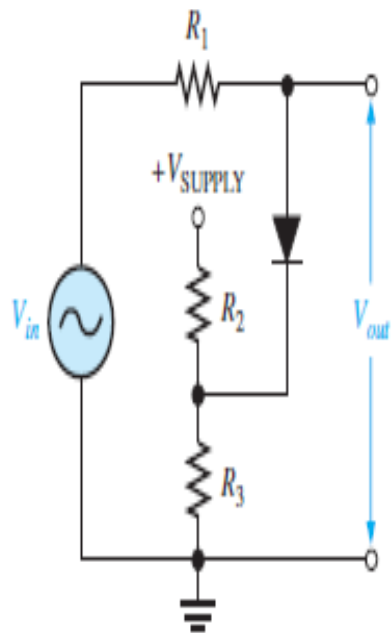
$$V_{\text{BIAS}} = \left(\frac{R_3}{R_2 + R_3} \right) V_{\text{SUPPLY}}$$



(a) Positive limiter

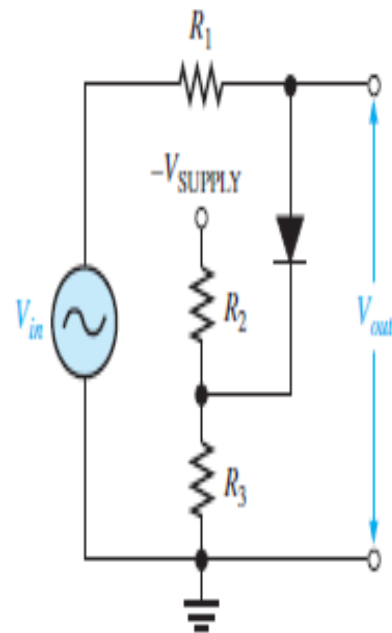

(b) Negative limiter

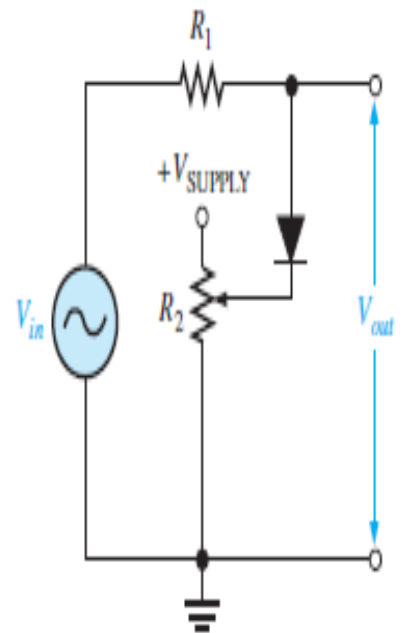


(c) Variable positive limiter

EXAMPLE 2-12

Describe the output voltage waveform for the diode limiter in Figure 2-61.

► **FIGURE 2-61**

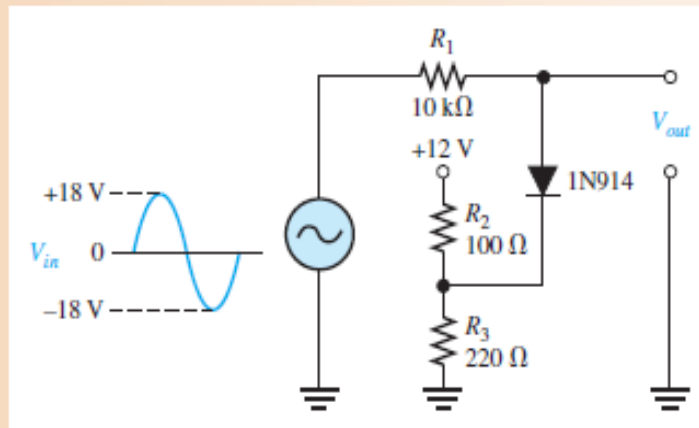


Solution The circuit is a positive limiter. Use the voltage-divider formula to determine the bias voltage.

$$V_{\text{BIAS}} = \left(\frac{R_3}{R_2 + R_3} \right) V_{\text{SUPPLY}} = \left(\frac{220 \, \Omega}{100 \, \Omega + 220 \, \Omega} \right) 12 \, \text{V} = 8.25 \, \text{V}$$


The output voltage waveform is shown in Figure 2-62. The positive part of the output voltage waveform is limited to $V_{\text{BIAS}} + 0.7 \, \text{V}$.

► **FIGURE 2-62**

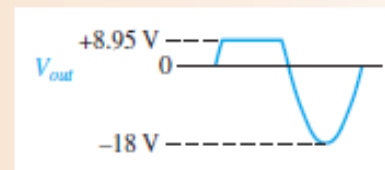


Diode Clampers

- A clamper adds a dc level to an ac voltage. **Clampers** are sometimes known as *dc restorers*.
- The operation of this circuit can be seen by considering the first negative half-cycle of the input voltage. When the input voltage initially goes negative, the diode is forward biased, allowing the capacitor to charge to near the peak of the input $V_{pin} - 0.7 \text{ V}$.
- Just after the negative peak, the diode is reverse-biased. This is because the cathode is held near $V_{pin} - 0.7 \text{ V}$ by the charge on the capacitor. The capacitor can only discharge through the high resistance of RL .

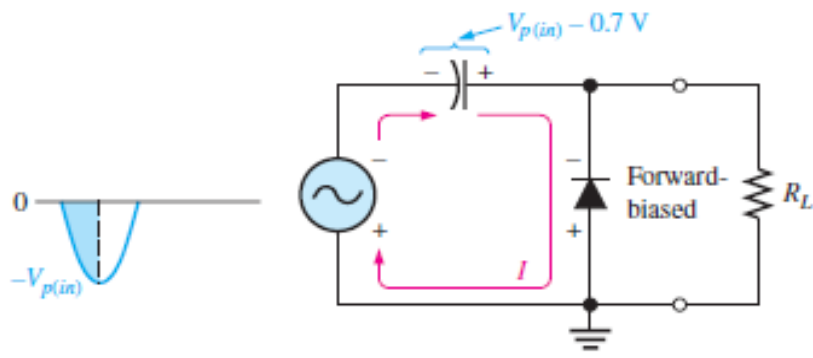


(a)

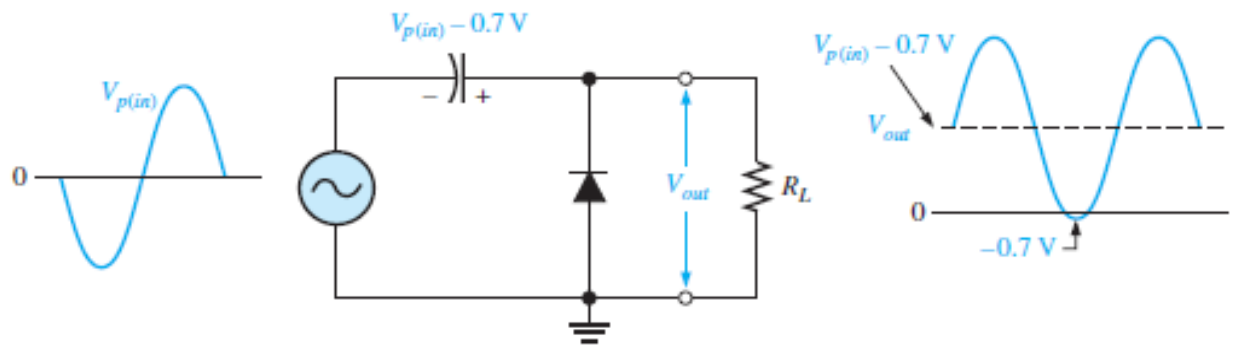

(b)

Negative Clampers


- If the diode is turned around, a negative dc voltage is added to the input voltage to produce the output voltage as shown in Figure

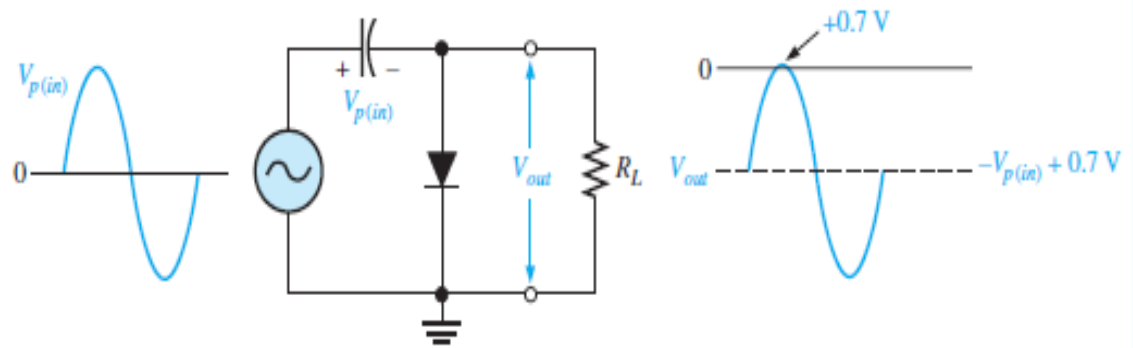

EXAMPLE 2-13

What is the output voltage that you would expect to observe across R_L in the clamping circuit of Figure 2-65? Assume that RC is large enough to prevent significant capacitor discharge.

► FIGURE 2-65

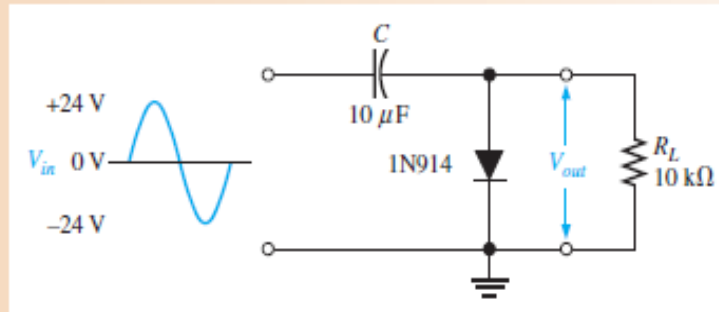


Solution Ideally, a negative dc value equal to the input peak less the diode drop is inserted by the clamping circuit.

$$V_{DC} \cong -(V_{p(in)} - 0.7 \text{ V}) = -(24 \text{ V} - 0.7 \text{ V}) = -23.3 \text{ V}$$

Actually, the capacitor will discharge slightly between peaks, and, as a result, the output voltage will have an average value of slightly less than that calculated above. The output waveform goes to approximately $+0.7 \text{ V}$, as shown in Figure 2-66.


► FIGURE 2-66

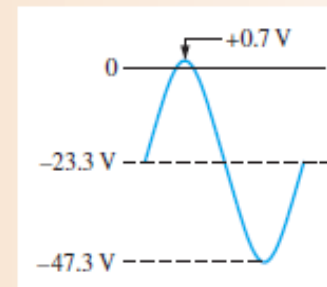Output waveform across R_L for Figure 2-65.




Homework:

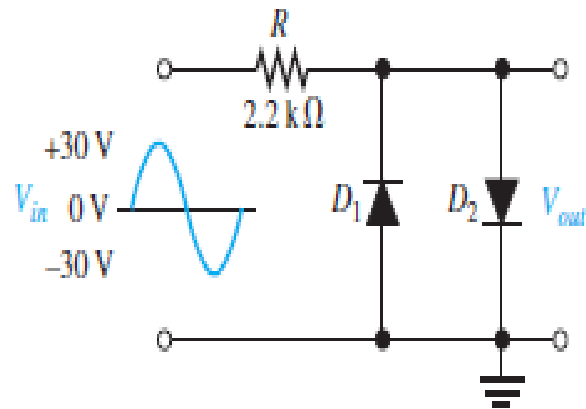- Determine and draw the output waveform of the following circuits



(a)

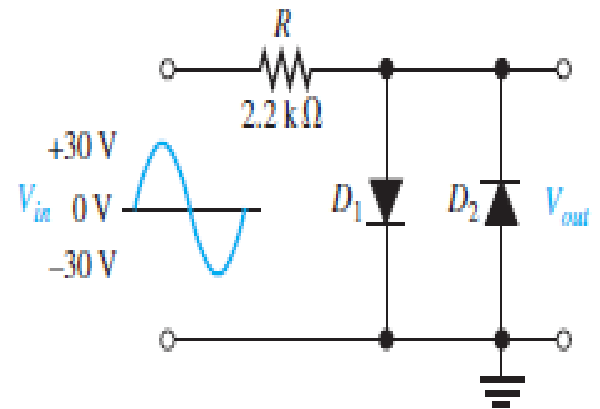

(b)



Thank you