

National University

Int. to Electrical Eng.

Circuit Theorem

Thevenin's Theorem

Introduction:


- The theorem was independently derived in 1853 by the German scientist [Hermann von Helmholtz](#) and in 1883 by [Léon Charles Thevenin's](#) (1857–1926), an [electrical engineer](#) with France's national [Postes et Télégraphes](#) telecommunications organization.

Thevenin's theorem holds that:

- Any linear electrical network containing only voltage sources, current sources and resistances can be replaced at terminals A-B by an equivalent combination of a voltage source V_{th} in a series connection with a resistance R_{th} .
- The equivalent voltage V_{th} is the voltage obtained at terminals A-B of the network with terminals A-B open circuited.
- The equivalent resistance R_{th} is the resistance that the circuit between terminals A and B would have if all ideal voltage sources in the circuit were replaced by a short circuit and all ideal current sources were replaced by an open circuit.


Continued:

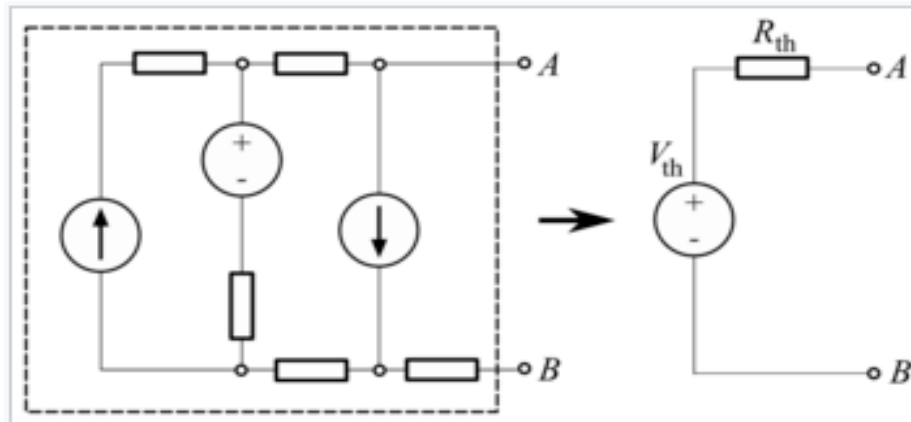- If terminals A and B are connected to one another, the current flowing from A to B will be V_{th}/R_{th} . This means that R_{th} could alternatively be calculated as V_{th} divided by the short-circuit current between A and B when they are connected together.



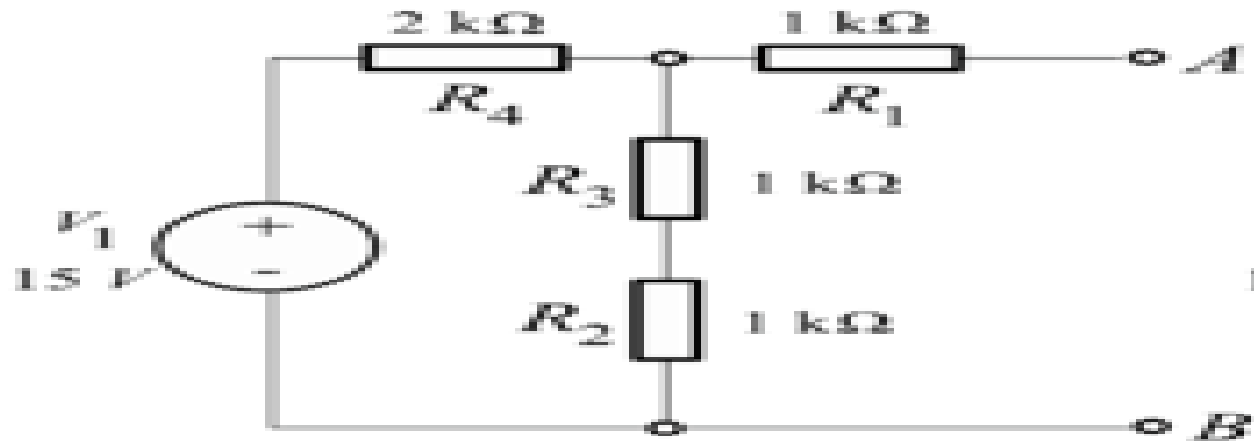
Example:

- Find Thevenin's equivalent circuit for the circuit below:




Solution:

- calculating the equivalent voltage:

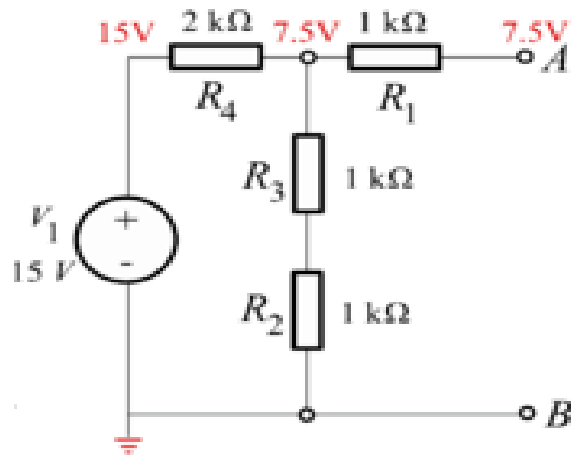

$$\begin{aligned} V_{\text{Th}} &= \frac{R_2 + R_3}{(R_2 + R_3) + R_4} \cdot V_1 \\ &= \frac{1\text{ k}\Omega + 1\text{ k}\Omega}{(1\text{ k}\Omega + 1\text{ k}\Omega) + 2\text{ k}\Omega} \cdot 15\text{ V} \\ &= \frac{1}{2} \cdot 15\text{ V} = 7.5\text{ V} \end{aligned}$$

- Calculating equivalent resistance:

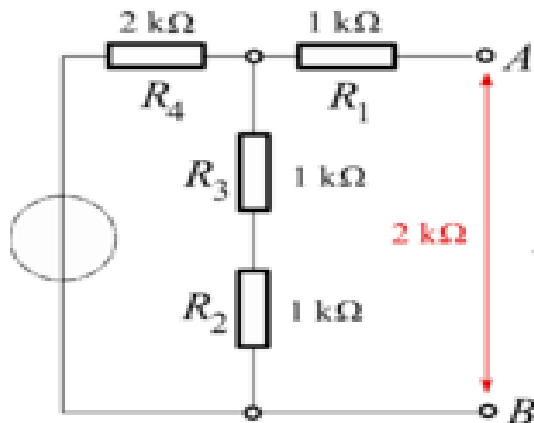

$$\begin{aligned}
 R_{\text{Th}} &= R_1 + [(R_2 + R_3) \parallel R_4] \\
 &= 1\text{ k}\Omega + [(1\text{ k}\Omega + 1\text{ k}\Omega) \parallel 2\text{ k}\Omega] \\
 &= 1\text{ k}\Omega + \left(\frac{1}{(1\text{ k}\Omega + 1\text{ k}\Omega)} + \frac{1}{(2\text{ k}\Omega)} \right)^{-1} = 2\text{ k}\Omega.
 \end{aligned}$$

Thevenin's equivalent circuit:

