

National University

Int. to Electrical Eng.

Circuit Theorem

Norton's Theorem

Introduction:


- Norton's theorem was independently derived in 1926 by [Siemens & Halske](#) researcher [Hans Ferdinand Mayer](#) (1895–1980) and [Bell Labs](#) engineer [Edward Lawry Norton](#) (1898–1983).

Norton theory hold that:


- Any linear electrical network with current sources and only resistances can be replaced at terminals $A-B$ by an equivalent current source I_{no} in parallel connection with an equivalent resistance R_{no} .
- This equivalent current I_{no} is the current obtained at terminals $A-B$ of the network with terminals $A-B$ short circuited.

Continued:

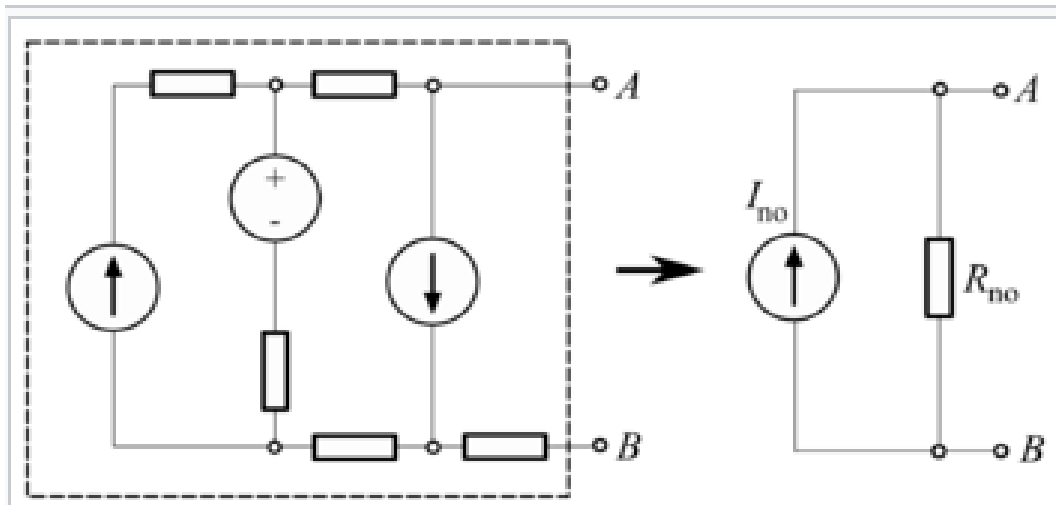- This equivalent resistance R_{no} is the resistance obtained at terminals A - B of the network with all its voltage sources short circuited and all its current sources open circuited



Norton equivalent circuit:

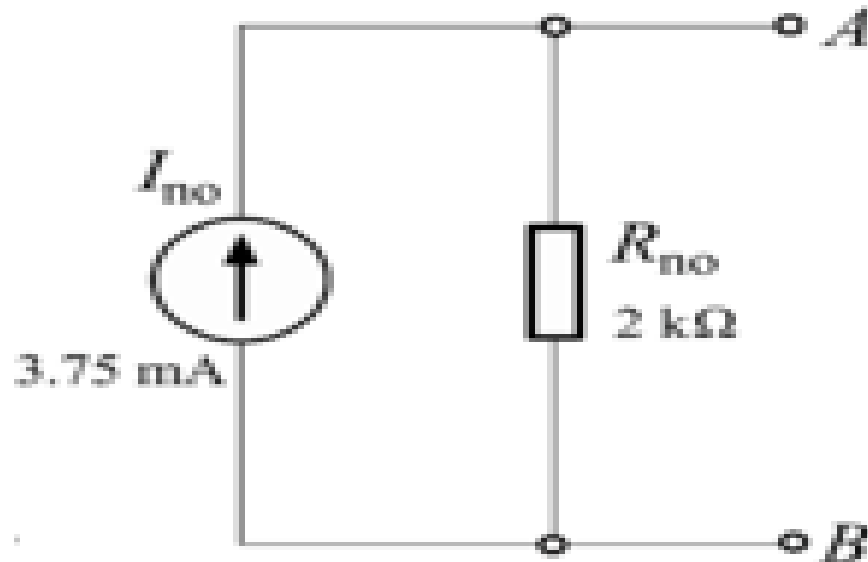

To find the equivalent:

1. Find the Norton current I_{no} . Calculate the output current, I_{AB} , with a short circuit as the load (meaning 0 resistance between A and B). This is I_{no} .
2. Find the Norton resistance R_{no} . When there are no dependent sources

Continued:


there are two methods of determining the Norton impedance R_{no} :

- Calculate the output voltage, V_{AB} , when in [open circuit](#) condition). R_{no} equals this V_{AB} divided by I_{no} .
- Or replace independent voltage sources with short circuits and independent current sources with open circuits. The total resistance across the output port is the Norton impedance R_{no} .

This is equivalent to calculating the Thevenin's resistance.

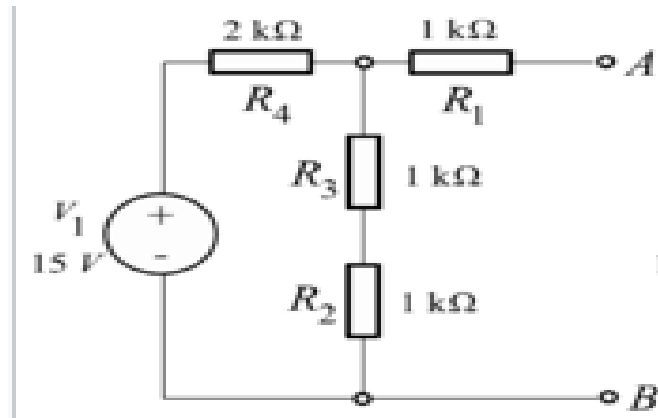Example:

- Find Norton equivalent circuit for the circuit below:




Solution:

- *the total current I_{total} is given by:*

$$I_{total} = \frac{15V}{2k\Omega + 1k\Omega \parallel (1k\Omega + 1k\Omega)} = 5.625\text{mA}.$$

The current through the load is then, using the [current divider rule](#):
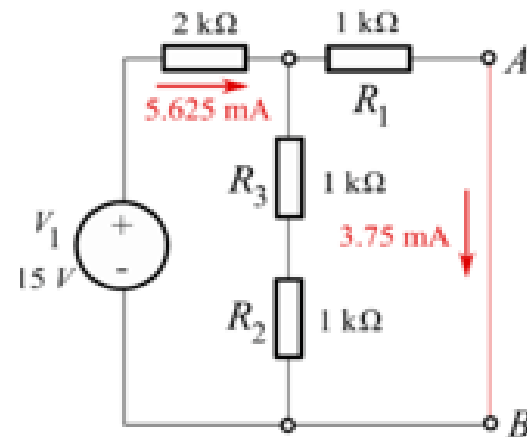
$$I_{no} = \frac{1k\Omega + 1k\Omega}{(1k\Omega + 1k\Omega + 1k\Omega)} \cdot I_{total}$$
$$= 2/3 \cdot 5.625\text{mA} = 3.75\text{mA}.$$




Continued:

And the equivalent resistance looking back into the circuit is:



$$R_{no} = 1\text{ k}\Omega + (2\text{ k}\Omega \parallel (1\text{ k}\Omega + 1\text{ k}\Omega)) = 2\text{ k}\Omega.$$

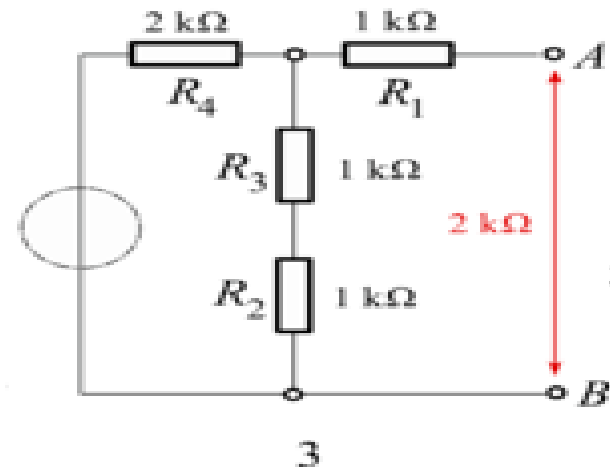So the equivalent circuit is a 3.75 mA current source in parallel with a 2 k Ω resistor.



Example:

Norton's Theorem

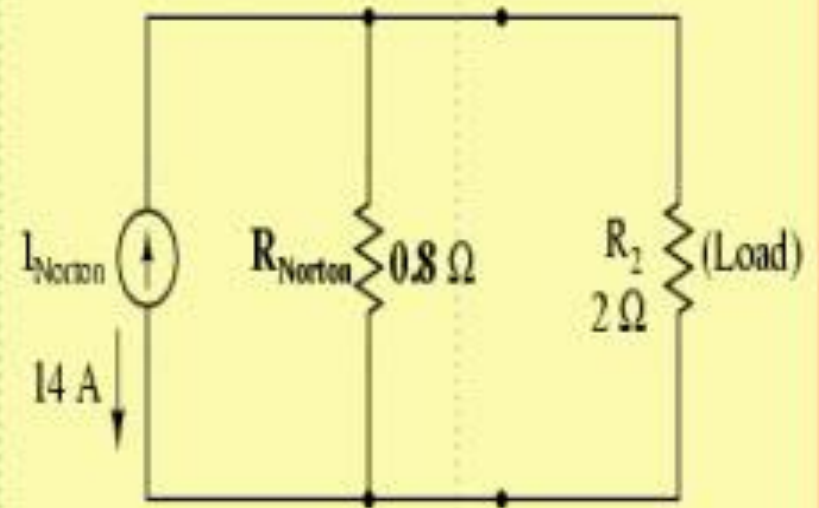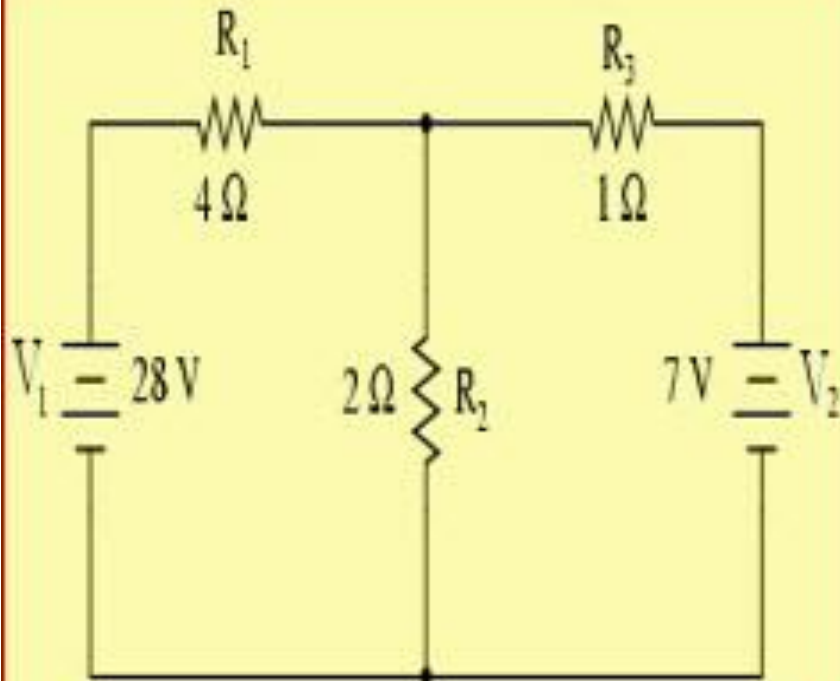

Example:

