

**National University**

**faculty of Engineering and  
Architecture**


**Maximum Power Transfer  
Theorem**

# Introduction:

- The Maximum Power Transfer Theorem can be defined as, a resistive load is connected to a DC-network, when the load resistance ( $R_L$ ) is equivalent to the internal resistance then it receives highest power is known as Thevenin's equivalent resistance of the source network.

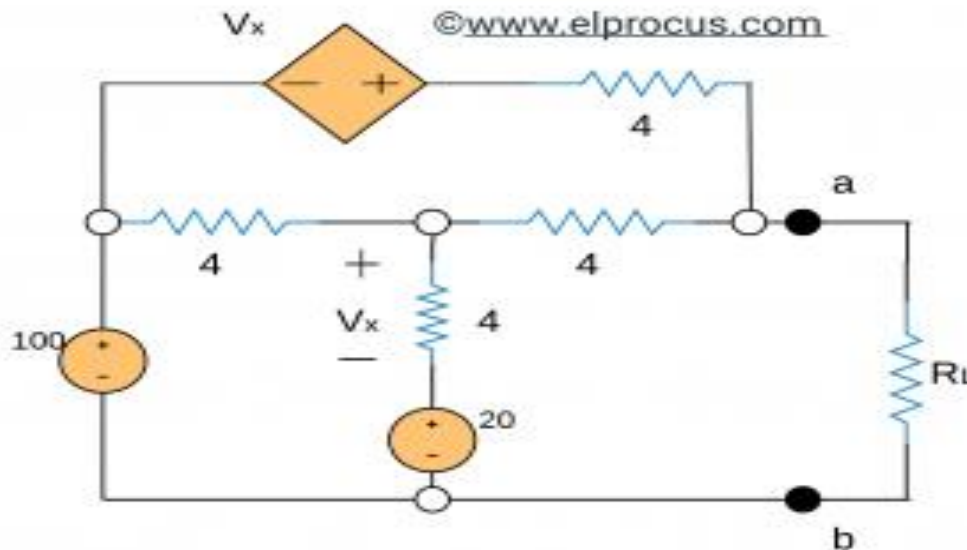
# Example:

Find the load resistance  $R_L$  that enables the circuit to deliver maximum power toward the load. Also, find the maximum power delivered to the load.


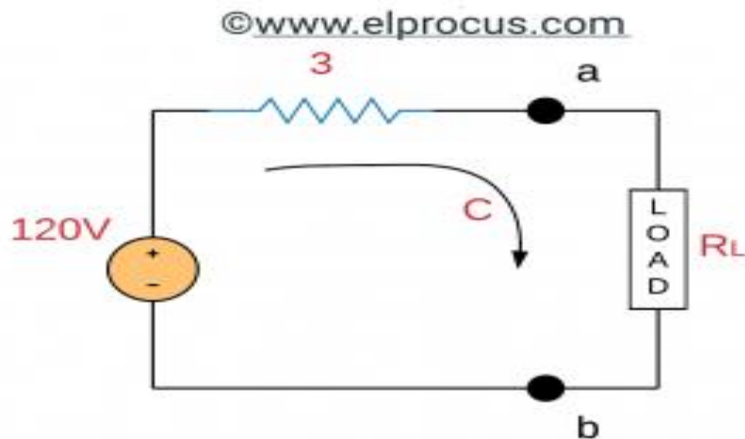
# Solution:

1- find the Thevenin's equivalent circuit using nodal analysis:



# Continue:

2-  $R_L = R_{th}$


3- the maximum power transferred to  $R_L$  is:

$$i^2 R_L = \left( \frac{120}{6} \right)^2 \cdot 3 = 1200 \text{ [W]}$$

# Example:

- Determine the maximum power that can be delivered to the variable resistor R.

©www.elprocus.com

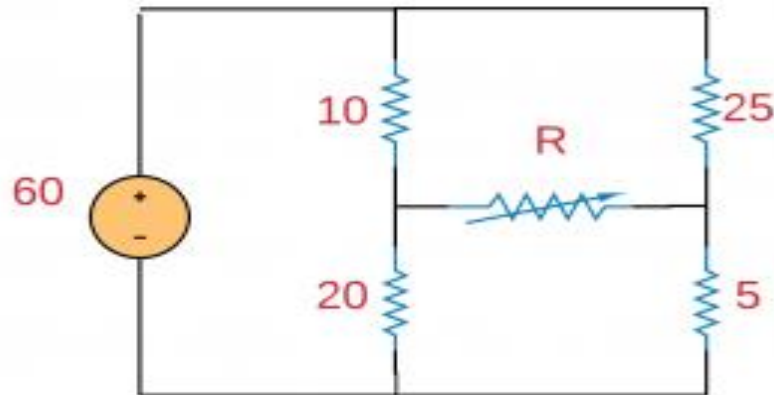

# Solution:

- 1- Thevenin's equivalent circuit:

